

Total No. of Questions : 5]

SEAT No. :

P210

[Total No. of Pages : 3

[4117]-22
F.Y. B.Sc.
ELECTRONIC SCIENCE
EL1-T2: Principles of Digital Electronics
(Paper - II) (2008 Pattern) (42220)

Time :3 Hours]

[Max. Marks :80

Instructions to the candidates:

- 1) *All questions are compulsory.*
- 2) *Neat labelled diagrams must be drawn wherever necessary.*
- 3) *Use of calculator & log table is allowed.*
- 4) *Figures to the right indicate full marks.*

Q1) Answer the following questions in brief :

[16]

- a) Convert
 $(123.746)_{10} = (?)_8$.
- b) What is positive and negative logic level?
- c) Simplify the following equation using laws of Boolean algebra.
$$Y = ABCD + ABC + AB + A\bar{B}$$
- d) State the difference between half adder circuit and full adder circuit?
- e) What is the function of strobe in Multiplexer?
- f) Draw logic diagram and write truth for T flip-flop.
- g) State the difference between Bipolar logic families and saturated Bipolar logic families.
- h) Define the following term associated with memory:
 - i) Address line.
 - ii) Data line.

Q2) Answer any four of the following :

[16]

- a)
 - i) Convert decimal number 37.2 into binary number.
 - ii) Convert
 $(E4)_{16} = (?)_8$.

P.T.O.

- b) Explain with neat diagram, how Ex-OR gate can be used as parity generator?
- c) Construct OR gate and NOT gate using NAND gates.
- d) Draw logic diagram for 4 bit universal adder. Explain the action with suitable example.
- e) What is decoder? Write short note on BCD to seven segment decoder?
- f) How will you get D and T flip flops from J.K flip flop? Draw logic diagram and truth table of each.

Q3) Answer any Four of the following : [16]

- a) Minimise the following expression using K-map

$$ABC + \overline{A}B\overline{C} + B$$
 and draw its simplified logic diagram.
- b) Draw logic diagram of half sub tractor. Write its truth table, explain.
- c) What do you mean by code converter? Explain encoder and decoder with suitable example.
- d) What is a decade counter? Which IC's can be used as decade counter?
- e) Draw the circuit of CMOS- NOR gate, explain its action.
- f) Explain the working of dynamic memory cell. Write the advantage and disadvantages of dynamic memory cell over static memory cell.

Q4) Answer any four of the following : [16]

- a) Construct logic circuit using AND, OR and NOT gate for the following Boolean expressions
 - i) $Y = (A + B) \cdot (\overline{A} + \overline{B})$
 - ii) $Y = (A + B) \cdot (\overline{C} + \overline{D}) \cdot (\overline{A} + C)$
- b) Explain Keyboard encoder with suitable diagram.
- c) Explain the working of parallel in serial out shift register?
- d) Define the terms the noise immunity and noise margin, Explain in brief.
- e) List the performance characteristics of digital integrated circuit. Explain worst case input output voltages.
- f) Explain the structural organization of memory chip with suitable example.

Q5) Answer any four of the following :

[16]

- a) i) What is excess-3 code?
ii) Draw logic diagram of 2 input OR gate using diode.
- b) i) State any two applications of shift register.
ii) Draw circuit of S-R flip-flop using two input logic gate. What are limitations of S-R flip-flop.
- c) i) Give the relation between number of output and select lines in multiplexer. Explain with example.
ii) What are types of seven segment display? Show internal connections of them?
- d) i) Why synchronous counters are faster in operation?
ii) State the function of IC's
A) IC 7447
B) IC 74153.
- e) i) CMOS logic family is better than bipolar family-comment.
ii) State the advantage of schottky TTL over TTL.
- f) i) Define terms Fan In and Fan Out.
ii) What is unipolar logic family? What are drawbacks of CMOS family?

www.puneqp.com ***