

# SYMBIOSIS INTERNATIONAL UNIVERSITY

(Established under Section 3 of the UGC Act, 1956 vide notification No. F.9-12/2001-U.3 of the Government of India)  
Accredited by NAAC with 'A' grade



Name of the Institute : SIT

Programme Name : B.Tech.

Batch : 2013-17, 12-16 & 11-15

Programme Code : 070121

Semester : III

Course Name : Digital Electronics and Logic Circuits (CS & IT)

Course Code : 0701211302, 0701213302

Date : 11/12/2014

Maximum Marks : 60

Day : Thursday

Time : 1.30 PM to 4.00 PM

## Instructions:

1. All questions are compulsory.
2. Draw diagrams and state assumptions wherever necessary.
3. Calculators are NOT allowed.

## PART A

- Q.1
- a. Convert the given number into the bases indicated.
    - i)  $(1010.11)_{10}$  into binary, hexadecimal. 2
    - ii)  $(77.7)_8$  into hexadecimal. 1
  - b. Subtract using 2's complement  $(3)_{10} - (7)_{10}$ . 3
  - c. Convert the following.
    - i)  $(1101)_{\text{gray}}$  into BCD. 1
    - ii)  $(1011)_{\text{BCD}}$  into gray code. 1
    - iii)  $(1011)_{\text{gray}}$  into BCD. 1
  - d. State the difference between TTL and CMOS with respect to fan-out, power dissipation per gate, propagation delay. 3
  - e. Compare Combinational and Sequential Circuits. 3

## PART B

- Q.2
- a. Draw and explain 2-input NAND TTL logic gate with totem pole output driver. 8
  - b. Simplify the following expressions using K-map: 3

$$Y = \pi_{ABCD} M(0, 2, 3, 4, 6, 8, 11, 13)$$

c. With the help of standard TTL logic family explain the following characteristics of digital integrated circuits.

- i) Noise margin
- ii) Propagation delay time

Q.3 a. Draw the circuit diagram and describe the operation performed by following circuits:

- i) Full Adder
- ii) Full Subtractor

b. Simplify the following expressions using Boolean laws:

- i)  $Y = (A+C)(A+D)(B+C)(B+D)$
- ii)  $Y = (B+BC)(B+\overline{B}C)(B+D)$

c. Draw logic diagram of clocked RS flip-flop and derive its characteristic equation.

Q.4 a. How will you convert the basic SR flip-flop into:

- i) JK flip-flop
- ii) T flip-flop

b. Perform the following operations in excess-3 code.

- i)  $(24)_{10} + (39)_{10}$
- ii)  $(3)_{10} - (8)_{10}$

c. Explain advantages and disadvantages of totem pole output.

OR

Q.4 a. Write Short Notes on

- i) 4- Bit magnitude comparator
- ii) Reflective property and advantages of Gray code.

b. Using K-map realize the following expression using minimum number of gates.

- i)  $Y = \sum_{PQRS} m(1,3,4,5,7,9,11,13,15)$
- ii)  $Y = \pi_{ABCD} M(0, 4, 5, 7, 10, 11, 14, 15)$